

TABLE OF CONTENTS

PREFACE	xvii
Part 1 BASIC CONCEPTS.....	1
1 Electronic Concepts	3
Current.....	3
Charge.....	5
Voltage.....	6
Direct and Alternating Voltage and Current	8
Harmonics	11
Measurement of AC Voltage or Current.....	12
Frequency, Rise/Fall Times, and Period.....	13
Frequency Measurement.....	16
Complex Waveforms (Fourier Analyses).....	18
Chapter Endnotes	23
Direction of Current Flow.....	23
Some Standard Symbols Used in Electronics	24
Some Fundamental Definitions.....	25
Important Names in Electronics	26
2 Propagation Times	27
Propagation Speed.....	27
Propagation Times	28
Trace Configurations and Signal Propagation.....	29
Circuit Timing Issues	32
Wavelength.....	35

3 Electrical Components	37
The Three Basics.....	37
Resistance.....	38
Ohm's Law.....	39
Capacitance.....	43
Charge Storage.....	47
Formula for Capacitance.....	48
Capacitance Functions and Effects.....	49
Inductance.....	50
Formulas for Inductance.....	55
Charge and Discharge Currents.....	56
Resonance.....	60
4 Voltage and Current Changes and Time Constants	63
Voltage and Current Changes Through Resistors.....	63
Voltage and Current Changes Through Capacitors.....	64
Voltage and Current Changes Through Inductors.....	66
Some Interesting Inductive Circuit Dynamics.....	69
Time Constants.....	71
A Note on Charge and Discharge Equations.....	76
5 Resistance	77
Kirchhoff's Laws.....	77
Series Resistors.....	79
Parallel Resistors.....	81
Voltage Dividers.....	83
Amplifier Feedback and Gain.....	85
Power.....	86
Equivalent Circuits.....	88
Power Curve.....	91
Power Sources.....	93
Conductance.....	94
6 Reactance	97
Capacitive Reactance.....	98
Inductive Reactance.....	99
Ohm's Law for Reactance.....	101
Series LC Combinations.....	104
Parallel LC Circuits.....	107
Resonance.....	111
Poles and Zeros.....	115

Susceptance 119

7 Impedance and Phase Shift.....121

 Impedance 121

 Effect of Frequency..... 128

 Another RC Example 129

 Classic RC Filter 131

 Combining Impedances 133

 Resonance and Q..... 134

 Series RLC Circuits..... 137

 Series RLC at Resonance 140

 Admittance 142

 Chapter Endnotes 144

 Detailed Calculations for Figure 7-8 144

 RLC Simulation 145

 Imaginary Numbers..... 146

Part 2 SIGNAL INTEGRITY ISSUES147

8 Signal Integrity Overview149

9 Electromagnetic Interference (EMI)155

 Background..... 155

 Fields and Cancellations..... 156

 Some Basic Truths..... 158

 Signal Coupling 159

 Loop Area..... 161

 Slots in Planes 1 162

 Return Pathways..... 163

 Power Plane Returns..... 164

 Changing Trace Layers..... 165

 Unrelated Planes..... 166

 Stripline..... 167

 Stubs..... 168

 Common Mode 169

 The 20-H Rule 173

 Picket Fences (Faraday Shields) 174

10 Reflections and Transmission Lines	175
Communications Model	175
Transmission Lines	178
Critical Length	181
Reflection Coefficients.....	183
Visualizing Reflections	184
Determining Trace Impedance.....	185
Termination Techniques.....	190
Parallel.....	192
Thevenin	192
AC Termination	194
Series	194
Diode	195
Some Design Issues.....	196
Changing Trace Layers 1	196
Power Planes.....	197
Changing Trace Layers 2.....	197
Slots in Planes 2.....	199
Stubs.....	200
Absolute vs. Relative Value of Z_0	201
Chapter Endnote.....	203
On Formulas	203
11 Some Transmission Line Simulations.....	207
Basic Simulation	207
Series Termination	215
Placement Issues	217
Branches, or Ys.....	219
12 Crosstalk.....	221
Forward versus Backward Crosstalk.....	221
Backward Crosstalk.....	223
Forward Crosstalk	225
In Summary	226
Estimating Crosstalk	226
Calculations	226
Coupling.....	227
Distance.....	227
Terminations.....	229
UltraCAD Calculator.....	230
HyperLynx Simulation Tool	231
Design Considerations.....	232

Slots in Planes 3	232
Guard Bands	233
13 Crosstalk Simulations	235
Basic Model.....	235
Add an Uncoupled Region.....	239
Effect of Length	240
Stripline.....	242
Stripline With Terminations	242
More Realistic Example	244
Summary	247
14 Differential Traces and Impedance	249
Background.....	249
Advantages	249
Key Assumptions	251
Design Rules.....	255
Design Rule 1 (Equal Length).....	255
Common Mode Implications.....	255
Differential Signals and Loop Areas.....	256
Design Rule 2 (Close Together).....	257
Rule 2 Consequence	258
Design Rule 3 (Differential Impedance).....	260
Differential Mode Impedance	260
Common Mode Impedance.....	261
Design Rule 4 (Constant Separation).....	262
Differential Simulations	262
Calculating Differential Impedance	265
Edge Coupled.....	266
Broadside Coupled	268
15 Bypass Caps and Decoupling Systems	269
Traditional Approach	269
Size and Quantity	273
Placement	275
Connection	276
Power System Impedance Approach	277
Ideal Response	277
Capacitor Response	278
Inductance Effects.....	278
Multiple Capacitors.....	280
Additional Capacitor Value	281

Planar Capacitance	282
Equivalent Series Resistance (ESR)	285
Self Resonant Frequencies	287
Effects of Multiple Capacitors	288
Parallel Capacitors.....	288
Resonance.....	290
Impedance at Self-Resonant Frequency	291
Impedance at Anti-Resonance	292
General Case Analysis.....	293
Consequences.....	294
Summary	296
16 Power Systems.....	297
Power Supply Voltages	297
Need For Power Planes	300
Strategies For Designing With Plane.....	300
Some Design Rules	303
Connecting Reference Planes Together	303
Overlapping Planes.....	304
Decoupling to Wrong Plane.....	305
Signals Crossing Separations.....	305
Stack-Ups	307
Conclusion.....	308
17 Lossy Lines and Eye Diagrams	311
Lossy Lines.....	311
Skin Effect	312
Dielectric Absorption	314
Lossy Line Model	314
Eye Diagrams.....	316
Equalization.....	318
Passive Equalization.....	319
Active Equalization	319
Summary	320
Part 3 Appendices, Glossary, and Index	323
Appendices	325
A UltraCAD's Square Wave Simulator.....	325
B Why Inductors Induct	329
C Logarithms.....	345

Table of Contents**xv**

D Phase Shift Simulation	351
E Complex Algebra.....	357
F Transmission Line Simulation.....	367
G Echo Illustration	369
H UltraCAD Freeware Calculators.....	371
I TDRs and VNAs.....	375
J Right Angle Corners.....	383
Glossary.....	387
Index.....	397
About the Author.....	403